

Experiment 5 Arithmetic Processor

1. Sequence assignment

$Op_2 Op_1$	Arithmetic Function
0 0	
0 1	
1 0	
1 1	

2. Processor Design

Construct the truth table for the input processor. (Use $a_i, b_i, 0, 1$)

$Op_2 Op_1$	x_i	y_i	c_0
00			
01			
10			
11			

Experiment 5 Arithmetic Processor

1. Sequence assignment

$Op_2 Op_1$	Arithmetic Function
0 0	$2B + 1$
0 1	$A - B$
1 0	$A + B$
1 1	$A - 1$

2. Processor Design

Construct the truth table for the input processor. (Use $a_i, b_i, 0, 1$)


$Op_2 Op_1$	x_i	y_i	c_0
00	b_i	b_i	1
01	a_i	b_i'	1
10	a_i	b_i	0
11	a_i	1	0

2. Processor Design

Construct the truth table for the input processor. (Use $a_i, b_i, 0, 1$)

$Op_2 Op_1$	x_i	y_i	c_0
00	b_i	b_i	1
01	a_i	b_i'	1
10	a_i	b_i	0
11	a_i	1	0

 Label the data inputs of the two 4-to-1 multiplexers given below for the realization of x_i, y_i .



Express the initial carry c_0 as a function of Op_2 and Op_1 .

$$c_0 =$$

2. Processor Design


Construct the truth table for the input processor. (Use $a_i, b_i, 0, 1$)

$Op_2 Op_1$	x_i	y_i	c_0
00	b_i	b_i	1
01	a_i	b_i'	1
10	a_i	b_i	0
11	a_i	1	0

Label the data inputs of the two 4-to-1 multiplexers given below for the realization of x_i, y_i .

Use the following signal names for input processor
1QD for a_i , 2QD for b_i ,
 $Op_2, Op_1, x_i, y_i, z_i$

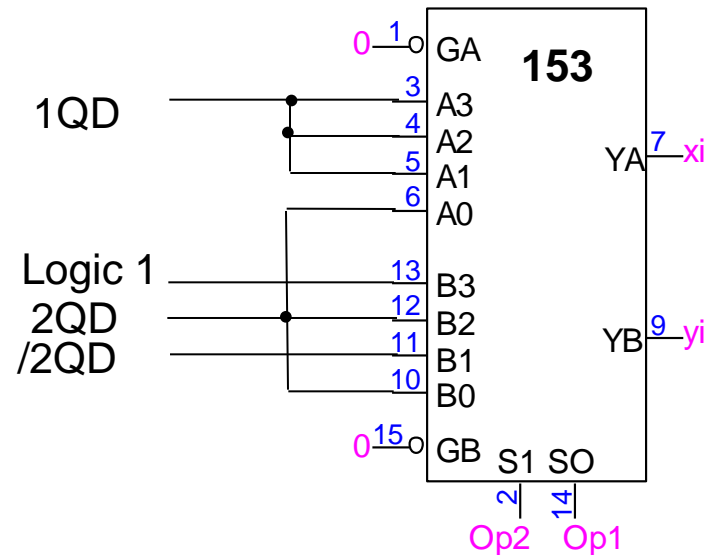Use the following signal names for control signals
 $1s1, 1s0, 2s1, 2s0, c_0, C_2, C_1$



Express the initial carry c_0 as a function of Op_2 and Op_1 .

$$c_0 = Op_2'$$

Construct the truth table for the control circuit.

State	START	$(s_1)_{R1}$	$(s_0)_{R1}$	$(s_1)_{R2}$	$(s_0)_{R2}$	C_2	C_1
T_0	0						
T_0	1						
T_1	d						
T_2	d						
T_3	d						
T_4	d						
T_5	d						

$(s_1)_{R1} =$


$(s_0)_{R1} =$

$(s_1)_{R2} =$

$(s_0)_{R2} =$


$C_2 =$

$C_1 =$





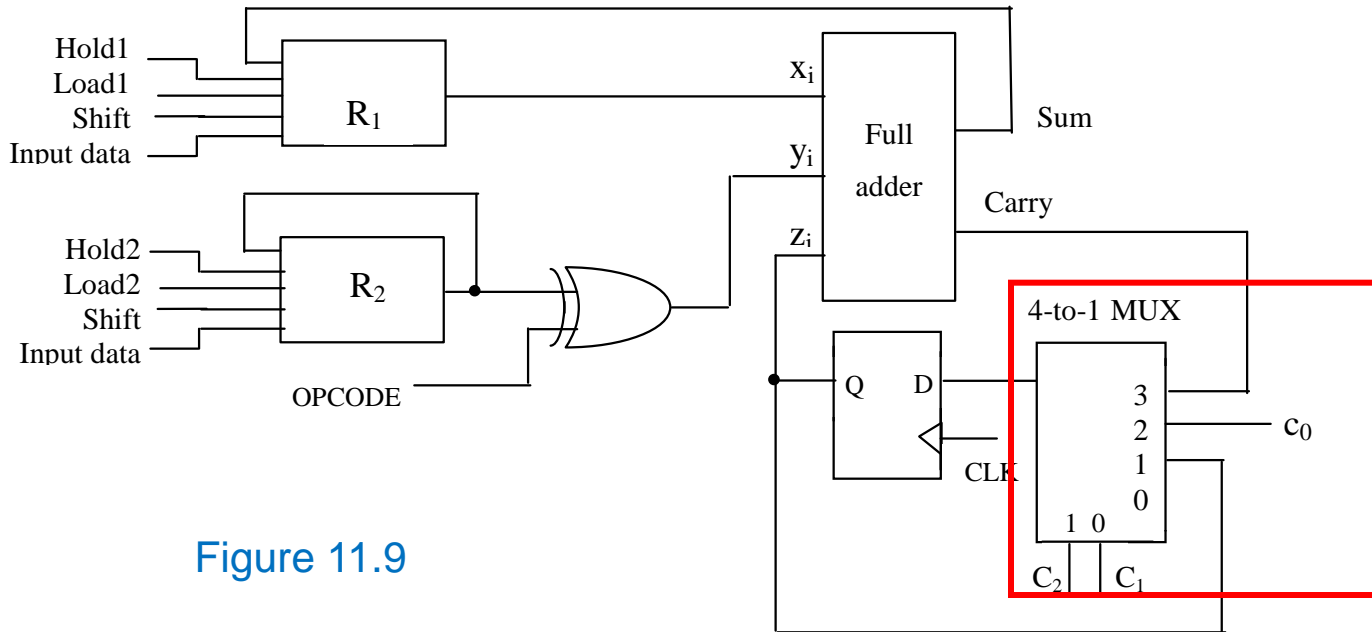


Note the difference in the data inputs of the two multiplexers.

Lab 5 schematic diagram







 


  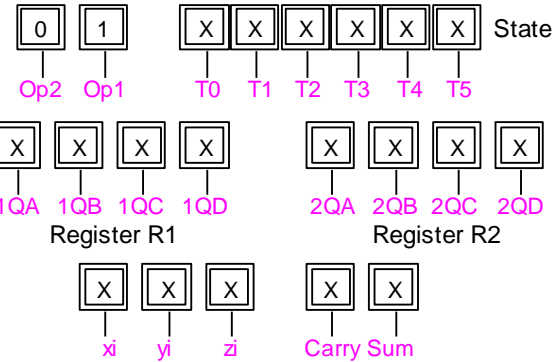  16.265 Logic Design
 Experiment 5: Arithmetic Processor
 Name:
 Student Logic Number:
 Function Set Number:




Use the following signal names for input processor
 1QD for ai, 2QD for bi,
 Op2, Op1, xi, yi, zi

       Use the following signal names for control signals
 1s1, 1s0, 2s1, 2s0, c0, C2, C1



IC#6

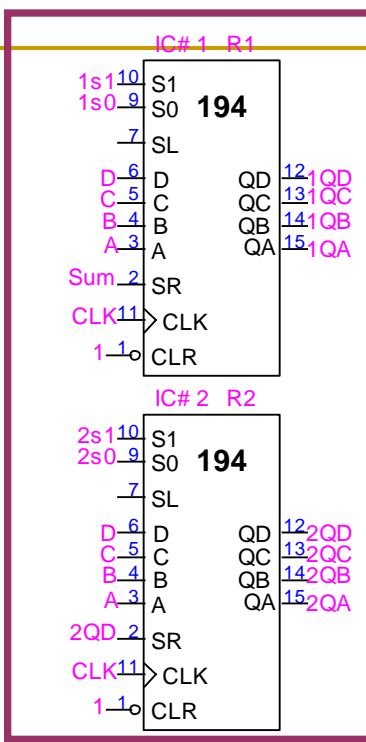

Use the following signal names for input processor
1QD for ai, 2QD for bi,
Op2, Op1, xi, yi, zi

Use the following signal names for control signals
1s1, 1s0, 2s1, 2s0, c0, C2, C1

